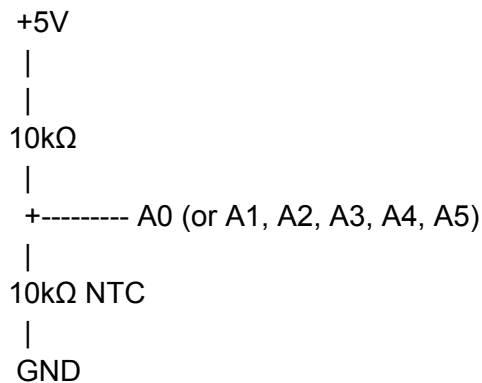


System Overview


- 6× identical temperature sensors
- Each sensor = 10k fixed resistor + 10k NTC thermistor
- Arduino reads **A0–A5**
- Arduino selects **coldest sensor**
- Output is **PWM on D9** (0–5V via filter if needed)

Wiring Diagram (Text / ASCII)


One Sensor (repeat for A0–A5)



All Sensors Combined

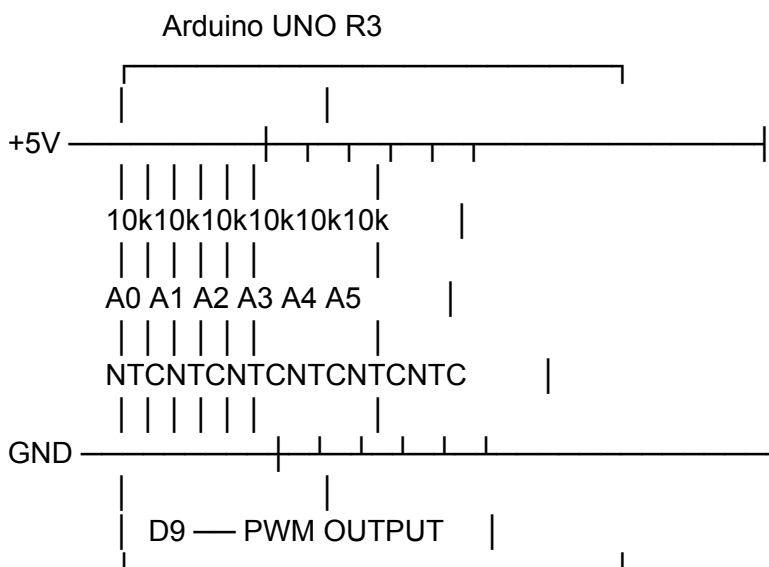

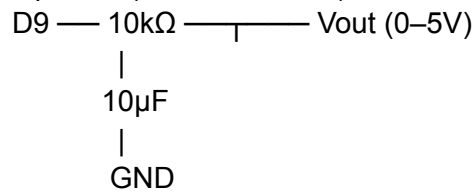Optional (Recommended): PWM Smoothing Filter



- ✓ Makes PWM behave like a real DAC
- ✓ Stable voltage for PLCs, comparators, or ADCs

Important Notes

- Each thermistor **MUST** have its own 10k resistor
- All grounds must be common
- Do **NOT** share junctions between sensors
- Use **20kΩ meter range** to verify components

Bill of Materials (per board)

Item	Qty
Arduino UNO R3	1
10k NTC Thermistor	6
10k 1% Resistor	6
0.1 μF Capacitor (optional, noise)	6
10 μF Capacitor (PWM filter)	1
Jumper wires	as needed

