

FULL WIRING DIAGRAM (text-based, exact)

(Optional noise filter)


Analog Signal + \longrightarrow Arduino A0
 Analog Signal GND \longrightarrow Arduino GND

markdown

A0 —||— GND
 0.1μF

2 PWM → Analog Filter (this is where your 10μF 50V cap goes)

SCSS

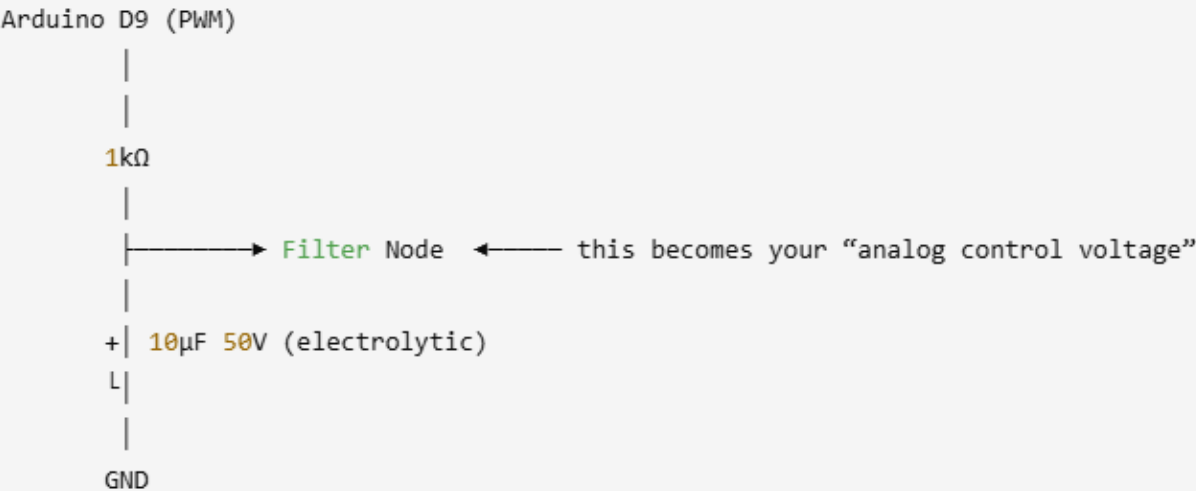

⚠ Cap polarity

- + → Filter Node
- - → GND

3 MOSFET (P30N06LE) Power Stage

Looking at the MOSFET from the front (text facing you, legs down):

ini

LEFT = Gate
 MIDDLE = Drain
 RIGHT = Source

Gate control

CSS

Filter Node $\xrightarrow{220\Omega}$ Gate (LEFT)
Gate (LEFT) $\xrightarrow{10k\Omega}$ GND

Load switching

SCSS

+5V External Supply \longrightarrow Load (+)
Load (-) \longrightarrow Drain (MIDDLE)
Source (RIGHT) \longrightarrow GND

⚡ VERY IMPORTANT: COMMON GROUND

All grounds must be connected together:

CSS


Arduino GND
External 5V Supply GND
Analog Signal GND
MOSFET Source

If grounds are not common \rightarrow it will NOT work correctly.

If your load is inductive (motor, solenoid, relay)

Add a flyback diode across the load:

pgsql

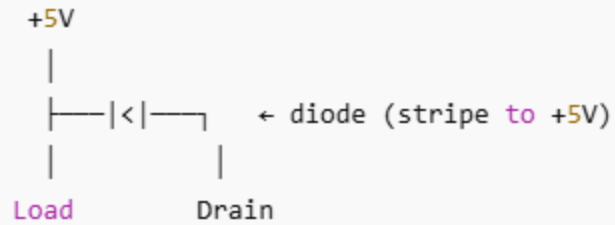

Examples:

- 1N5819 (preferred)
- 1N4007 (OK for slow loads)